

LAB 6 – Raja Aadhithan

Design – Sequence Detector:

Code:

```
module seq_det(input seq_in,clock,reset,output det_o);
reg [1:0]state,next_state;
parameter IDLE=2'b00, STATE1 = 2'b01, STATE2 = 2'b10, STATE3=2'b11;

always@(posedge clock)begin
    if(reset)begin
        state<=IDLE;
    end
    else begin
        state<=next_state;
    end
end
always@(*)begin
    case(state)
        IDLE : next_state = seq_in ? STATE1 : IDLE ;
        STATE1 : next_state = seq_in ? STATE1 : STATE2 ;
        STATE2 : next_state = seq_in ? STATE3 : IDLE ;
        STATE3 : next_state = seq_in ? STATE1 : STATE2 ;
        default: next_state=IDLE;
    endcase
end
assign det_o = (state==STATE3);
endmodule
```

Testbench:

```
module seq_det_tb();

    //Testbench global variables
    reg din,clock,reset;
    wire dout;

    //Parameter constant for CYCLE
    parameter CYCLE = 10;

    //DUT Instantiation
    seq_det SQD(.seq_in(din),
        .clock(clock),
        .reset(reset),
        .det_o(dout));

    //Step1 : Generate clock, using parameter "CYCLE"
    always
    begin
        #(CYCLE/2);
        clock = 1'b0;
        #(CYCLE/2);
        clock=~clock;
    end

    /*Step2 : Write a task named "initialize" to initialize
    the input din of sequence detector*/
    task initialize( );
        begin
            din = 0;
        end
    endtask

endmodule
```

```

//Delay task
task delay(input integer i);
    begin
        #i;
    end
endtask

/*Step3 : Write a task named "RESET" to reset the design,
use delay task for adding delays*/
//Reset task
task RESET();
    begin
        delay(5);
        reset=1'b1;
        delay(10);
        reset=1'b0;
    end
endtask

/*Step4 : Write a task named "stimulus" which provides input to
design on negedge of clock*/
task stimulus(input data);
    begin
        @(negedge clock);
        din = data;
    end
endtask


//Process to monitor the changes in the variables
initial
    $monitor("Reset=%b, state=%b, Din=%b, Output Dout=%b",
        reset,SQD.state,din,dout);

/*Process to display a string after the sequence is detected and dout is asserted.
SQD.state is used here as a path hierarchy where SQD is the instance name acting
like a handle to access the internal register "state" */
always@(SQD.state or dout)
    begin
        if(SQD.state==2'b11 && dout==1)
            $display("Correct output at state %b", SQD.state);
        end

/*Process to generate stimulus by calling the tasks and
passing the sequence in an overlapping mode*/
initial
    begin
        initialize;
        RESET;
        stimulus(0);
        stimulus(1);
        stimulus(0);
        stimulus(1);
        stimulus(0);
        stimulus(1);
        stimulus(1);
        RESET;
        stimulus(1);
        stimulus(0);
        stimulus(1);
        stimulus(1);
        delay(10);
        $finish;
    end
endmodule

```


Wave:

 

Output:

```
VSIM 41> run -all
# Reset=x, state=xx, Din=0, Output Dout=x
# Reset=1, state=xx, Din=0, Output Dout=x
# Reset=1, state=00, Din=0, Output Dout=0
# Reset=0, state=00, Din=0, Output Dout=0
# Reset=0, state=00, Din=1, Output Dout=0
# Reset=0, state=01, Din=1, Output Dout=0
# Reset=0, state=01, Din=0, Output Dout=0
# Reset=0, state=10, Din=0, Output Dout=0
# Reset=0, state=10, Din=1, Output Dout=0
# Correct output at state 11
# Reset=0, state=11, Din=1, Output Dout=1
# Reset=0, state=11, Din=0, Output Dout=1
# Reset=0, state=10, Din=0, Output Dout=0
# Reset=0, state=10, Din=1, Output Dout=0
# Correct output at state 11
# Reset=0, state=11, Din=1, Output Dout=1
# Reset=1, state=00, Din=1, Output Dout=0
# Reset=0, state=01, Din=1, Output Dout=0
# Reset=0, state=01, Din=0, Output Dout=0
# Reset=0, state=10, Din=0, Output Dout=0
# Reset=0, state=10, Din=1, Output Dout=0
# Correct output at state 11
# Reset=0, state=11, Din=1, Output Dout=1
# Reset=0, state=01, Din=1, Output Dout=0
# ** Note: $finish : C:/Users/Aadhithan/Documents/Vi
6/tb/seq_det_tb.v(117)
# Time: 135 ps Iteration: 0 Instance: /seq_det_tb
- -
```

RTL:

 

Design : Vending machine:

Code:

```
module coin(input clk,rst,i,j, output x,y);
parameter idle = 3'b000, st1 = 3'b001, st2 = 3'b010, st3 = 3'b011, st4 = 3'b100;
reg[2:0]next_state,state;
always@(*)begin
    case(state)
        idle : next_state = i ? ( j ? st2 : st1) : idle ;
        st1  : next_state = i ? ( j ? st3 : st2) : st1 ;
        st2  : next_state = i ? ( j ? st4 : st3) : st2 ;
        st3  : next_state = idle;
        st4  : next_state = idle;
        default: next_state = idle;
    endcase
end
always@(posedge clk or posedge rst)begin
    if(rst) state<=idle;
    else state<=next_state;
end
assign x = (state==st3)||(state==st4);
assign y = (state==st4);
endmodule
```

Testbench:


```
module coin_tb();
reg clk,reset,i,j;
wire x,y;
coin dut(clk,reset,i,j,x,y);
initial begin
    clk = 1;
    forever #5 clk = ~clk;
end
initial begin
    $monitor("@time:%3d,input (ij) is %b,%b and output (xy) is %b,%b",$time,i,j,x,y);
    reset = 1 ;
    #15;
    reset = 0;
    i = 0;
    j = 1;
    #10;
    i = 0;
    j = 0;
    #10;
    i = 1;
    j = 1;
    #10;
    i = 1;
    j = 0;
    #10;
    i = 0;
    j = 1;
    #10;
    i = 1;
    j = 1;
    #10;
    i = 1;
    j = 1;
    #10;
    i = 1;
    j = 0;
    #10;
end
```

```

i = 1;
j = 1;
#10;
i = 1;
j = 0;
#10;
i = 0;
j = 1;
#10;
i = 1;
j = 1;
#10;
i = 1;
j = 1;
#10;
i = 1;
j = 0;
#10;
$finish;
end
endmodule

```

Wave:

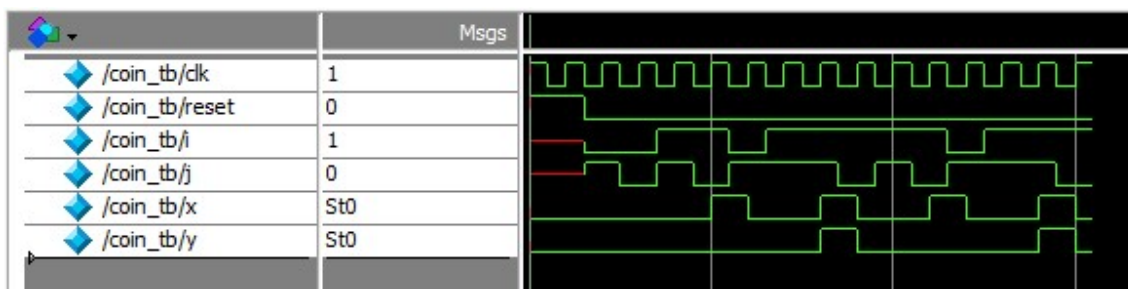

Output:

```

VSIM 45> run -all
# @time: 0,input (ij) is x,x and output (xy) is 0,0
# @time: 15,input (ij) is 0,1 and output (xy) is 0,0
# @time: 25,input (ij) is 0,0 and output (xy) is 0,0
# @time: 35,input (ij) is 1,1 and output (xy) is 0,0
# @time: 45,input (ij) is 1,0 and output (xy) is 0,0
# @time: 50,input (ij) is 1,0 and output (xy) is 1,0
# @time: 55,input (ij) is 0,1 and output (xy) is 1,0
# @time: 60,input (ij) is 0,1 and output (xy) is 0,0
# @time: 65,input (ij) is 1,1 and output (xy) is 0,0
# @time: 80,input (ij) is 1,1 and output (xy) is 1,1
# @time: 85,input (ij) is 1,0 and output (xy) is 1,1
# @time: 90,input (ij) is 1,0 and output (xy) is 0,0
# @time: 95,input (ij) is 1,1 and output (xy) is 0,0
# @time:105,input (ij) is 1,0 and output (xy) is 0,0
# @time:110,input (ij) is 1,0 and output (xy) is 1,0
# @time:115,input (ij) is 0,1 and output (xy) is 1,0
# @time:120,input (ij) is 0,1 and output (xy) is 0,0
# @time:125,input (ij) is 1,1 and output (xy) is 0,0
# @time:140,input (ij) is 1,1 and output (xy) is 1,1
# @time:145,input (ij) is 1,0 and output (xy) is 1,1
# @time:150,input (ij) is 1,0 and output (xy) is 0,0
# ** Note: $finish      : C:/Users/Aadhithan/Documents/Ve:
#   Time: 155 ps  Iteration: 0  Instance: /coin_tb
# 1

```

RTL:

