

## LAB 1 – Raja Aadhithan

Design - Full adder using Half adder:

Code:

```
module half_adder(input a,b,
                  output sum,carry);

    //Understand the Data-flow abstraction
    assign sum  = a ^ b;
    assign carry = a & b;

endmodule
```

```
module full_adder( input a_in,
                  b_in,
                  c_in,
                  output sum_out,
                  carry_out);

wire w1,w2,w3;

half_adder ha1(.a(a_in), .b(b_in), .sum(w1), .carry(w2));
half_adder ha2(.a(c_in), .b(w1), .sum(sum_out), .carry(w3));
or or1(carry_out, w2,w3);

endmodule
```

Test bench:

```
module full_adder_tb();

    //Testbench global variables
    reg  a,b,cin;
    wire sum,carry;

    //Variable for loop iteration
    integer i;

    //Step1 : Instantiate the full adder with order based port mapping
    full_adder DUT(a,b,cin,sum,carry);

endmodule
```

```

//Process to initialize the variables at 0ns
initial
begin
    a    = 1'b0;
    b    = 1'b0;
    cin = 1'b0;
end

//Process to generate stimulus using for loop
initial
begin
    for (i=0;i<8;i=i+1)
        begin
            {a,b,cin}=i;
            #10;
        end
    end


//Process to monitor the changes in the variables
initial
    $monitor("Input a=%b, b=%b, c=%b, Output sum =%b, carry=%b",a,b,cin,sum,carry);

//Process to terminate simulation after 100ns
initial #100 $finish;

endmodule

```

Wave:

 


Output:

```

# Input a=0, b=0, c=0, Output sum =0, carry=0
# Input a=0, b=0, c=1, Output sum =1, carry=0
# Input a=0, b=1, c=0, Output sum =1, carry=0
# Input a=0, b=1, c=1, Output sum =0, carry=1
# Input a=1, b=0, c=0, Output sum =1, carry=0
# Input a=1, b=0, c=1, Output sum =0, carry=1
# Input a=1, b=1, c=0, Output sum =0, carry=1
# Input a=1, b=1, c=1, Output sum =1, carry=1

```

RTL:

 

## Exercises:

Design : Ripple adder

Code:

```
module ripple_adder(input [3:0] a,b, input cin,
                   output[3:0] sum,output carry);
    wire [2:0] w;

    full_adder FA1(a[0],b[0],cin,sum[0],w[0]);
    full_adder FA2(a[1],b[1],w[0],sum[1],w[1]);
    full_adder FA3(a[2],b[2],w[1],sum[2],w[2]);
    full_adder FA4(a[3],b[3],w[2],sum[3],carry);
endmodule
```

Test bench:

```
module ripple_adder_tb();
    reg [3:0]a,b;
    reg c;
    wire [3:0]s;
    wire cy;
    integer i;
    initial begin
        a=0;
        b=0;
        c=0; end

    ripple_adder DUT(a,b,c,s,cy);
    initial begin
        for (i=0;i<16;i=i+1)
            begin
                a=i;
                b=i;
                c=!c;
                #10;
            end
        end
    initial
        $monitor("Input a=%b, b=%b, c=%b, Output sum =%b, carry=%b",a,b,c,s,cy);

        //Process to terminate simulation after 100ns
        initial #100 $finish;

endmodule
```

Wave:

+	/ripple_adder_tb/a	1001	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001
+	/ripple_adder_tb/b	1001	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001
	/ripple_adder_tb/c	0										
+	/ripple_adder_tb/s	0010	0001	0010	0101	0110	1001	1010	1101	1110	0001	0010
	/ripple_adder_tb/cy	St1										
+	/ripple_adder_tb/i	9	0	1	2	3	4	5	6	7	8	9


Output:

```

VSIM 28> run -all
# Input a=0000, b=0000, c=1, Output sum =0001, carry=0
# Input a=0001, b=0001, c=0, Output sum =0010, carry=0
# Input a=0010, b=0010, c=1, Output sum =0101, carry=0
# Input a=0011, b=0011, c=0, Output sum =0110, carry=0
# Input a=0100, b=0100, c=1, Output sum =1001, carry=0
# Input a=0101, b=0101, c=0, Output sum =1010, carry=0
# Input a=0110, b=0110, c=1, Output sum =1101, carry=0
# Input a=0111, b=0111, c=0, Output sum =1110, carry=0
# Input a=1000, b=1000, c=1, Output sum =0001, carry=1
# Input a=1001, b=1001, c=0, Output sum =0010, carry=1
# ** Note: $finish      : C:/Users/Aadhithan/Documents/Verilog_labs/lab1/sim/ripple_ad
der_tb.v(26)
#   Time: 100 ps  Iteration: 0  Instance: /ripple_adder_tb

```

RTL:

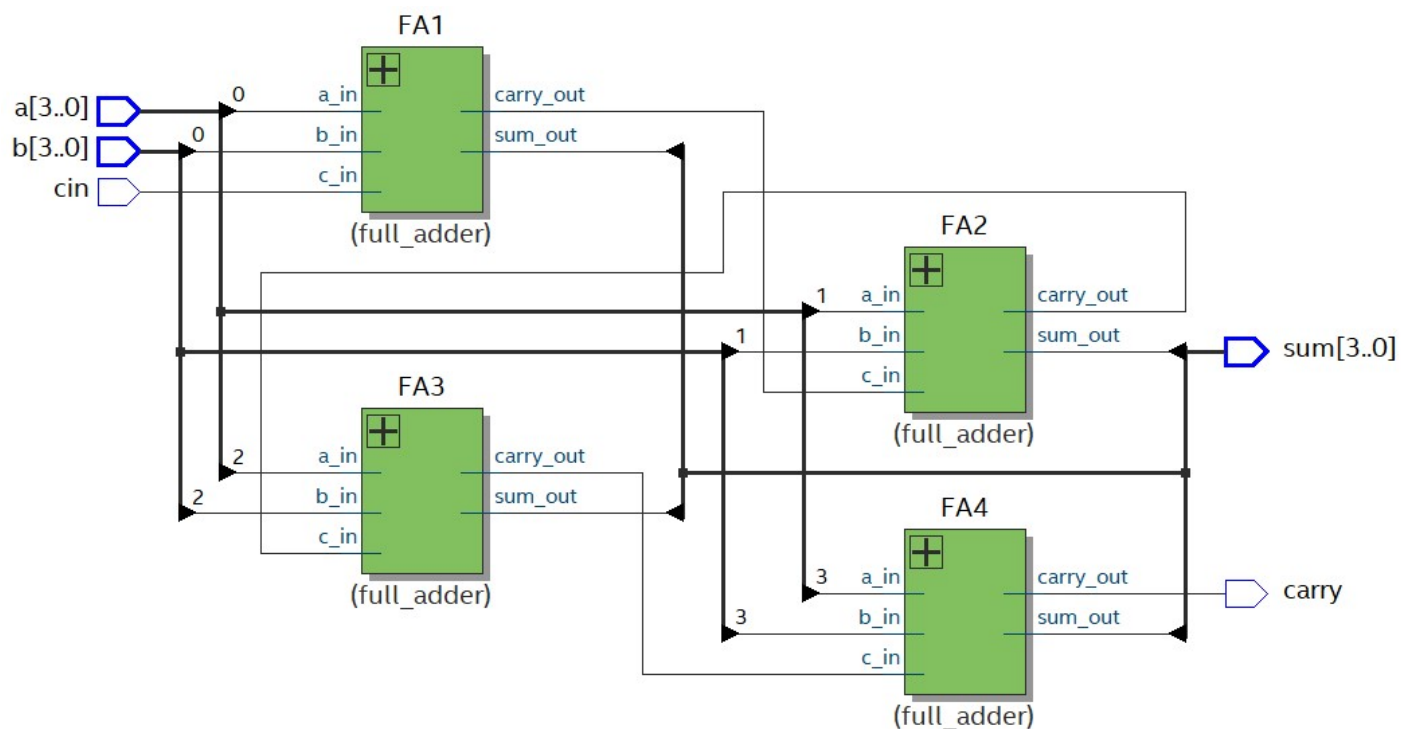

## Design : 4:1 mux using 2:1 mux

Code:


```
module mux2(input a,b,s, output x);
assign x = s ? b : a;
endmodule
```

```
module mux4(input a,b,c,d,s1,s2,output x);
wire w1,w2;
mux2 mu1(a,b,s2,w1);
mux2 mu2(c,d,s2,w2);
mux2 mu3(w1,w2,s1,x);
endmodule
```

Test bench:

```
module mux4_tb();
reg a,b,c,d,s1,s2;
wire x;
integer i;
mux4 DUT(a,b,c,d,s1,s2,x);
initial begin
    a=0;b=0;c=0;d=0;s1=0;s2=0;
end
initial begin
    for(i=0;i<64;i=i+1)
    begin
        {s1,s2,a,b,c,d}=i;
        #10;
    end
end
end
initial #1000 $finish;
endmodule
```

Wave:

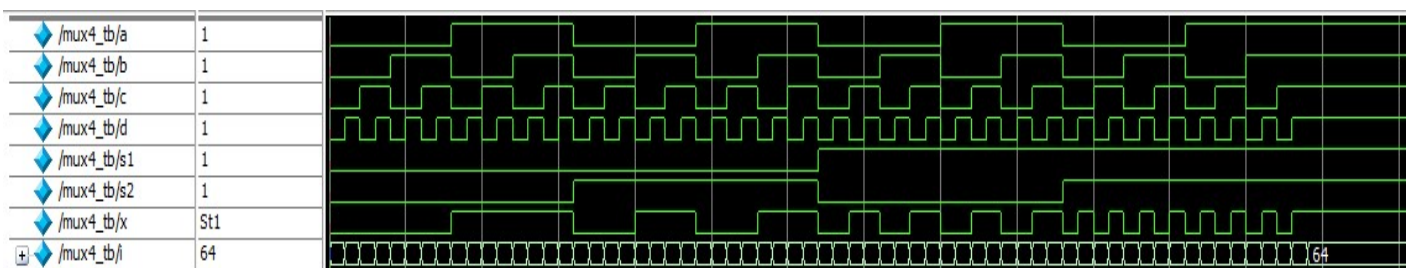

## Output:

```
VSIM 34> run -all
# @time: 0- selset is 00 nad input is 0,0,0,0 for output is 0
# @time: 10- selset is 00 nad input is 0,0,0,1 for output is 0
# @time: 20- selset is 00 nad input is 0,0,1,0 for output is 0
# @time: 30- selset is 00 nad input is 0,0,1,1 for output is 0
# @time: 40- selset is 00 nad input is 0,1,0,0 for output is 0
# @time: 50- selset is 00 nad input is 0,1,0,1 for output is 0
# @time: 60- selset is 00 nad input is 0,1,1,0 for output is 0
# @time: 70- selset is 00 nad input is 0,1,1,1 for output is 0
# @time: 80- selset is 00 nad input is 1,0,0,0 for output is 1
# @time: 90- selset is 00 nad input is 1,0,0,1 for output is 1
# @time:100- selset is 00 nad input is 1,0,1,0 for output is 1
# @time:110- selset is 00 nad input is 1,0,1,1 for output is 1
# @time:120- selset is 00 nad input is 1,1,0,0 for output is 1
# @time:130- selset is 00 nad input is 1,1,0,1 for output is 1
# @time:140- selset is 00 nad input is 1,1,1,0 for output is 1
# @time:150- selset is 00 nad input is 1,1,1,1 for output is 1
# @time:160- selset is 01 nad input is 0,0,0,0 for output is 0
# @time:170- selset is 01 nad input is 0,0,0,1 for output is 0
# @time:180- selset is 01 nad input is 0,0,1,0 for output is 0
# @time:190- selset is 01 nad input is 0,0,1,1 for output is 0
# @time:200- selset is 01 nad input is 0,1,0,0 for output is 1
# @time:210- selset is 01 nad input is 0,1,0,1 for output is 1
# @time:220- selset is 01 nad input is 0,1,1,0 for output is 1
# @time:230- selset is 01 nad input is 0,1,1,1 for output is 1
# @time:240- selset is 01 nad input is 1,0,0,0 for output is 0
# @time:250- selset is 01 nad input is 1,0,0,1 for output is 0
# @time:260- selset is 01 nad input is 1,0,1,0 for output is 0
# @time:270- selset is 01 nad input is 1,0,1,1 for output is 0
# @time:280- selset is 01 nad input is 1,1,0,0 for output is 1
# @time:290- selset is 01 nad input is 1,1,0,1 for output is 1
# @time:300- selset is 01 nad input is 1,1,1,0 for output is 1
# @time:310- selset is 01 nad input is 1,1,1,1 for output is 1
# @time:320- selset is 10 nad input is 0,0,0,0 for output is 0
# @time:330- selset is 10 nad input is 0,0,0,1 for output is 0
```




```

# @time:330- selstc is 10 nad input is 0,0,0,1 for output is 0
# @time:340- selstc is 10 nad input is 0,0,1,0 for output is 1
# @time:350- selstc is 10 nad input is 0,0,1,1 for output is 1
# @time:360- selstc is 10 nad input is 0,1,0,0 for output is 0
# @time:370- selstc is 10 nad input is 0,1,0,1 for output is 0
# @time:380- selstc is 10 nad input is 0,1,1,0 for output is 1
# @time:390- selstc is 10 nad input is 0,1,1,1 for output is 1
# @time:400- selstc is 10 nad input is 1,0,0,0 for output is 0
# @time:410- selstc is 10 nad input is 1,0,0,1 for output is 0
# @time:420- selstc is 10 nad input is 1,0,1,0 for output is 1
# @time:430- selstc is 10 nad input is 1,0,1,1 for output is 1
# @time:440- selstc is 10 nad input is 1,1,0,0 for output is 0
# @time:450- selstc is 10 nad input is 1,1,0,1 for output is 0
# @time:460- selstc is 10 nad input is 1,1,1,0 for output is 1
# @time:470- selstc is 10 nad input is 1,1,1,1 for output is 1
# @time:480- selstc is 11 nad input is 0,0,0,0 for output is 0
# @time:490- selstc is 11 nad input is 0,0,0,1 for output is 1
# @time:500- selstc is 11 nad input is 0,0,1,0 for output is 0
# @time:510- selstc is 11 nad input is 0,0,1,1 for output is 1
# @time:520- selstc is 11 nad input is 0,1,0,0 for output is 0
# @time:530- selstc is 11 nad input is 0,1,0,1 for output is 1
# @time:540- selstc is 11 nad input is 0,1,1,0 for output is 0
# @time:550- selstc is 11 nad input is 0,1,1,1 for output is 1
# @time:560- selstc is 11 nad input is 1,0,0,0 for output is 0
# @time:570- selstc is 11 nad input is 1,0,0,1 for output is 1
# @time:580- selstc is 11 nad input is 1,0,1,0 for output is 0
# @time:590- selstc is 11 nad input is 1,0,1,1 for output is 1
# @time:600- selstc is 11 nad input is 1,1,0,0 for output is 0
# @time:610- selstc is 11 nad input is 1,1,0,1 for output is 1
# @time:620- selstc is 11 nad input is 1,1,1,0 for output is 0
# @time:630- selstc is 11 nad input is 1,1,1,1 for output is 1
# ** Note: $finish      : C:/Users/Aadhithan/Documents/Verilog_labs/lab1/4_2_mux/muv4_
tb.v(16)
#   Time: 1 ns  Iteration: 0  Instance: /mux4_tb
# 1

```

RTL:

 




## Assignment:

Design: RTL for full adder.

Code:

```
module dataflow_fulladder(input a,b,c,d,s2,s1, output x);  
assign x = s1 ? (s2 ? d : c) : (s2 ? b : a );  
endmodule
```

RTL:

 


Design: 2x4 decoder.

Code:

```
module decoder(  
    input [1:0] in,  
    output [3:0] out  
);  
    assign out[0] = (~in[1] & (~in[0])) ;  
    assign out[1] = ( in[1] & (~in[0])) ;  
    assign out[2] = (~in[1] & ( in[0])) ;  
    assign out[3] = ( in[1] & ( in[0])) ;  
endmodule
```

RTL:

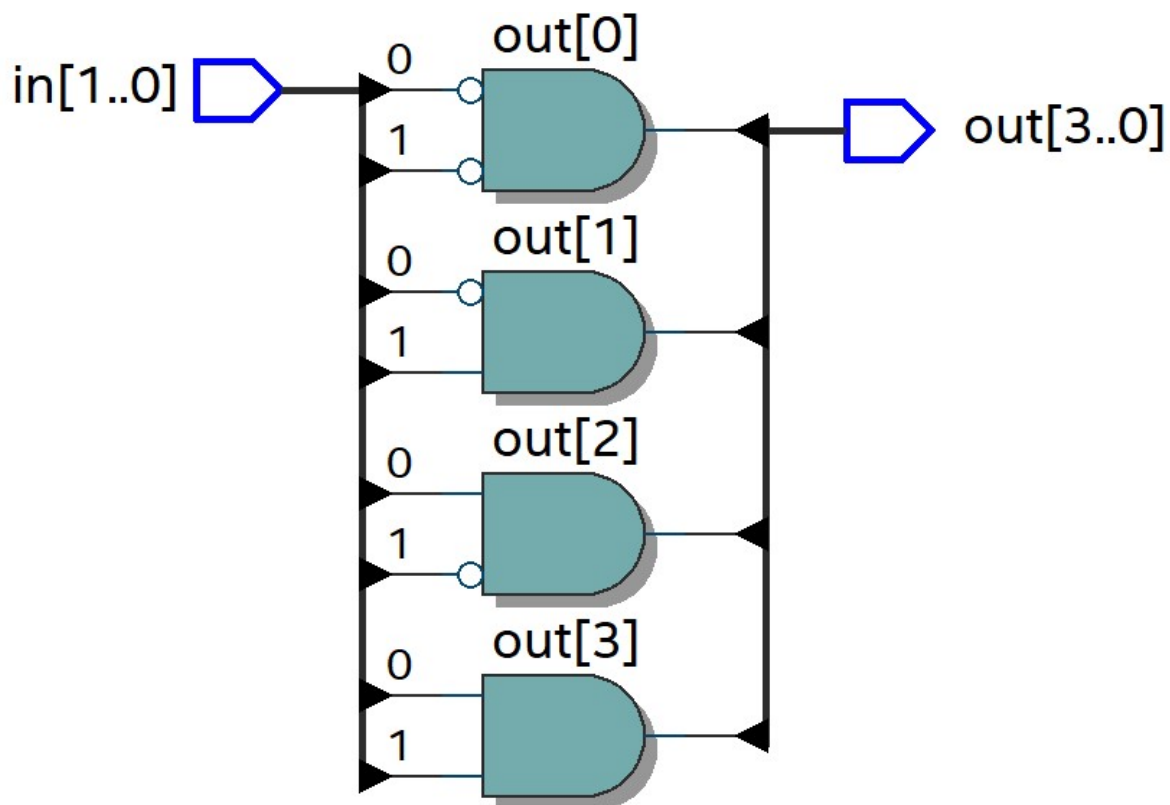

Design: 8x3 priority encoder.

Code:

```
module encoder(input [7:0]in , output [2:0] out);
wire[4:0] x;
wire[5:0] n;
not(n[5],in[5]);
not(n[4],in[4]);
not(n[3],in[3]);
not(n[2],in[6]);
not(n[1],in[2]);
or(out[2],in[7],in[6],in[5],in[4]);
and(x[0],in[3],n[5],n[4]);//!5,!4,3
and(x[1],n[5],n[4],n[3],in[2]);//!5,!4,!3,2
and(x[2],x[0],n[2]);//!6,!5,!4,3
and(x[3],n[2],in[5]);//!6,5
and(x[4],n[2],n[5],n[4],n[3],n[1],in[1]);//!6,!5,!4,!3,!2,1
or(out[1],in[7],in[6],x[0],x[1]);
or(out[0],in[7],x[3],x[4],x[2]);
endmodule
```

Test bench:

```
module encoder_tb();
reg [7:0] x;
wire [2:0] y;
integer i;
encoder dat(x,y);
initial begin
    for(i=0; i<8; i = i+1)
        begin
            x = 2**i;
            #10;
            x=2*i;
            #10;
        end
$finish;
end

initial $monitor("@ time: %3dps the input is %8b output is %3b",$time,x,y);

endmodule
```

Wave:

	Msgs	
/encoder_tb/x	000...	00000001 00000000 00000010 00000100 00001000 00000110
/encoder_tb/y	011	000 001 010 011 010
/encoder_tb/i	8	0 1 2 3

	Msgs	
/encoder_tb/x	000...	00001000 00000110 00010000 00001000 00100000 00001010 01000000 00001100 10000000 00000110
/encoder_tb/y	011	011 010 100 011 101 011 110 011 111 011
/encoder_tb/i	8	3 4 5 6 7


Output:

```

VSIM 38> run -all
# @ time: 0ps the input is 00000001 output is 000
# @ time: 10ps the input is 00000000 output is 000
# @ time: 20ps the input is 00000010 output is 001
# @ time: 40ps the input is 00000100 output is 010
# @ time: 60ps the input is 00001000 output is 011
# @ time: 70ps the input is 00000110 output is 010
# @ time: 80ps the input is 00010000 output is 100
# @ time: 90ps the input is 00001000 output is 011
# @ time: 100ps the input is 00100000 output is 101
# @ time: 110ps the input is 00001010 output is 011
# @ time: 120ps the input is 01000000 output is 110
# @ time: 130ps the input is 00001100 output is 011
# @ time: 140ps the input is 10000000 output is 111
# @ time: 150ps the input is 00001110 output is 011
# ** Note: $finish : C:/Users/Aadhithan/Documents/Verilog_labs/lab1/encoder/encoder_tb.v(14)
# Time: 160 ps Iteration: 0 Instance: /encoder_tb

```

RTL:

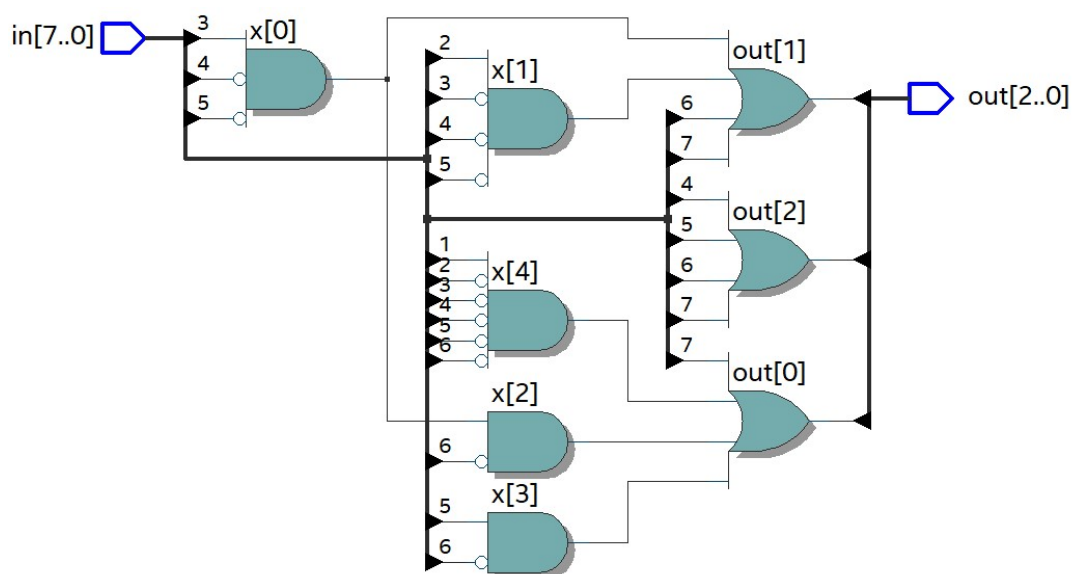

Design: 4x1 mux.


Code:

```
module mux_dec(input A,B,C,D, input [1:0] in, output Y);
wire [3:0] out;
reg x;
  assign out[0] = (~in[1]) & (~in[0]) ;
  assign out[1] = ( in[1]) & (~in[0]) ;
  assign out[2] = (~in[1]) & ( in[0]) ;
  assign out[3] = ( in[1]) & ( in[0]) ;
  always@(*)begin
    case(in)
      2'b00:x <= out[0] ? A : 1'bz;
      2'b01:x <= out[2] ? B : 1'bz ;
      2'b10:x <= out[1] ? C : 1'bz ;
      2'b11:x <= out[3] ? D : 1'bz ;
    endcase
  end
  assign Y = x;
endmodule
```


Test bench:

```
module mux4_tb();
reg a,b,c,d;
reg [1:0] s;
wire x;
integer i;
mux_dec DUT(a,b,c,d,s,x);
initial begin
  a=0;b=0;c=0;d=0;s = 0;
end
initial begin
  for(i=0;i<64;i=i+1)
    begin
      {s,a,b,c,d}=i;
      #10;
    end
end
initial #1000 $finish;
endmodule
```

Wave:

 

RTL:

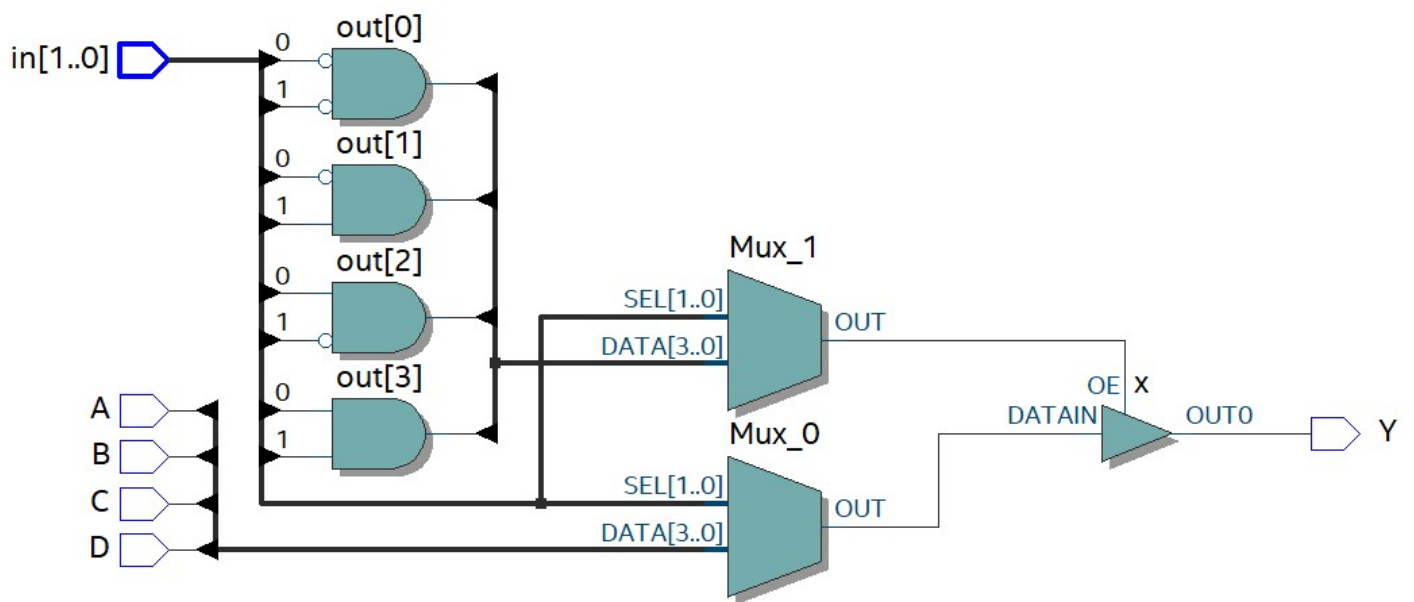



## Design: Bidirectional buffer


Code:

```
module bufer(inout a,b, input c);  
  bufif1(b,a,c);  
  bufif0(a,b,c);  
endmodule
```

Testbench:

```
module bufer_tb();  
  wire a,b;  
  reg c,ta,tb;  
  integer i;  
  bufer dut(a,b,c);  
  initial begin  
    for(i=0;i<8;i=i+1)  
    begin  
      {ta,tb,c}=i[2:0];  
      #10;  
    end  
  end  
  assign a = c ? ta : 1'bz;  
  assign b = c ? 1'bz : tb;  
endmodule
```

Wave:

 

## Output:

```
VSIM 49> run -all
# @time = 0: The value of a is 0 and b is 0
# enable is 0
# output ar is 0 and br is z
# @time = 10: The value of a is 0 and b is 0
# enable is 1
# output ar is z and br is 0
# @time = 20: The value of a is 0 and b is 1
# enable is 0
# output ar is 1 and br is z
# @time = 30: The value of a is 0 and b is 1
# enable is 1
# output ar is z and br is 0
# @time = 40: The value of a is 1 and b is 0
# enable is 0
# output ar is 0 and br is z
# @time = 50: The value of a is 1 and b is 0
# enable is 1
# output ar is z and br is 1
# @time = 60: The value of a is 1 and b is 1
# enable is 0
# output ar is 1 and br is z
# @time = 70: The value of a is 1 and b is 1
# enable is 1
# output ar is z and br is 1
# @time = 80: The value of a is 0 and b is 0
# enable is 0
# output ar is 0 and br is z
# @time = 90: The value of a is 0 and b is 0
# enable is 1
# output ar is z and br is 0
# @time = 100: The value of a is 0 and b is 1
# enable is 0
# output ar is 1 and br is z
# @time = 110: The value of a is 0 and b is 1
# enable is 1
# output ar is z and br is 0
# @time = 120: The value of a is 1 and b is 0
# enable is 0
# output ar is 0 and br is z
# @time = 130: The value of a is 1 and b is 0
# enable is 1
# output ar is z and br is 1
# @time = 140: The value of a is 1 and b is 1
# enable is 0
# output ar is 1 and br is z
# @time = 150: The value of a is 1 and b is 1
# enable is 1
# output ar is z and br is 1
```

## RTL:

